


Kirchhoff's Rules

Matthew Kirby

University of Arizona


PHYS 103 - Lecture 5

Internal Resistance

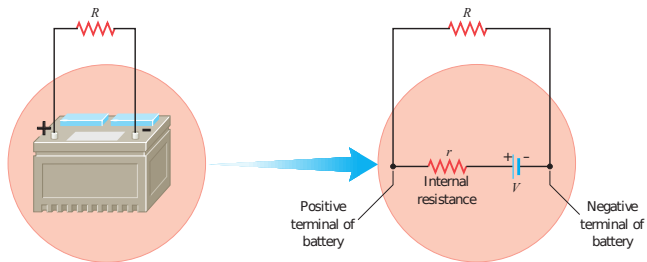


- In real batteries the voltage between the two terminals is not actually equal to the emf, \mathcal{E} , of the battery.

Internal Resistance

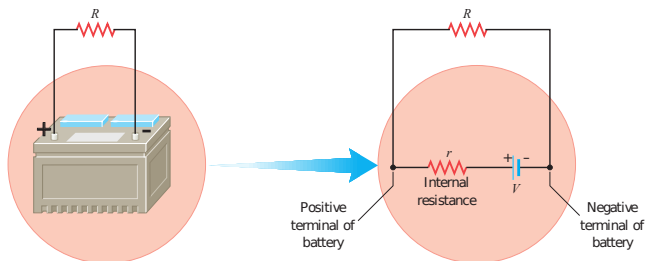


- In real batteries the voltage between the two terminals is not actually equal to the emf, \mathcal{E} , of the battery.
- A real battery will have a small resistance due to its internal structure.

Internal Resistance

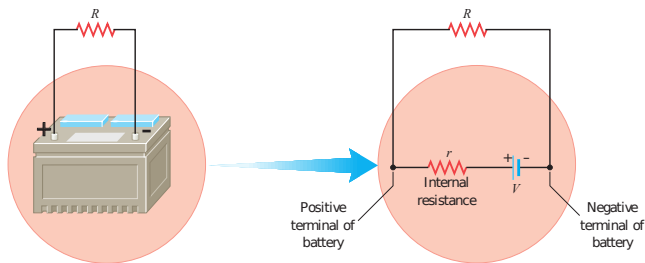

- In real batteries the voltage between the two terminals is not actually equal to the emf, \mathcal{E} , of the battery.
- A real battery will have a small resistance due to its internal structure.
- Typically very small, around the order of $r \sim 0.001 \Omega$.


Internal Resistance

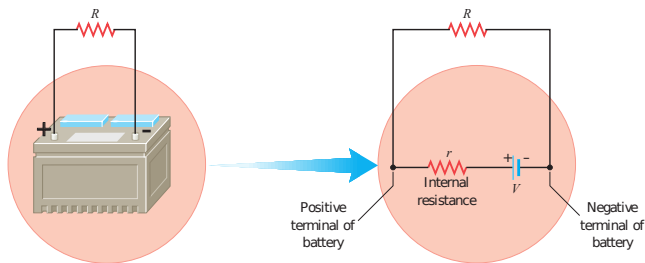

- In real batteries the voltage between the two terminals is not actually equal to the emf, \mathcal{E} , of the battery.
- A real battery will have a small resistance due to its internal structure.
- Typically very small, around the order of $r \sim 0.001 \Omega$.
- We can model this internal resistance as a resistor that will be in series with the rest of the circuit.

Real battery and two resistors in series

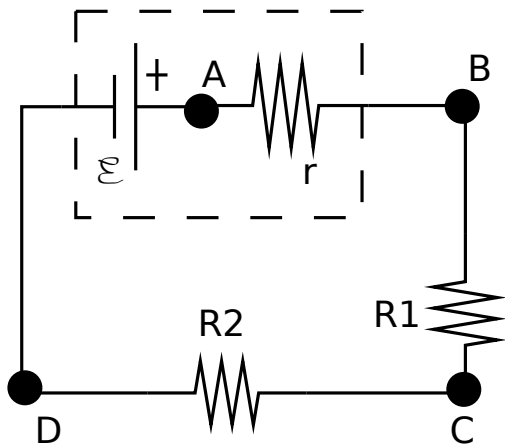
For the next few questions consider the circuit below containing a real battery with emf \mathcal{E} and internal resistance r . Beyond the battery, there are two resistors with resistances R_1 and R_2



Q: Real battery and two resistors in series I

Where would you define $V \equiv 0$?

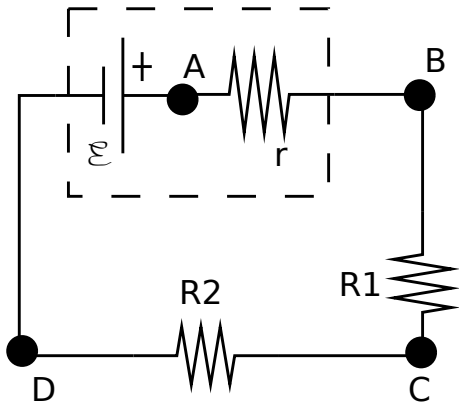
- (A) A
- (B) B
- (C) C
- (D) D
- (E) Infinitely far away from the battery



A: Real battery and two resistors in series I

Where would you define $V \equiv 0$?


- (A)
- (B)
- (C)
- (D) **D**
- (E)

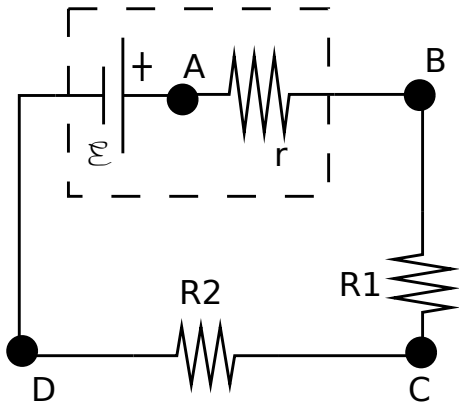

Q: Real battery and two resistors in series II

Given that definition of $V = 0$, at what point is the electric potential the largest?

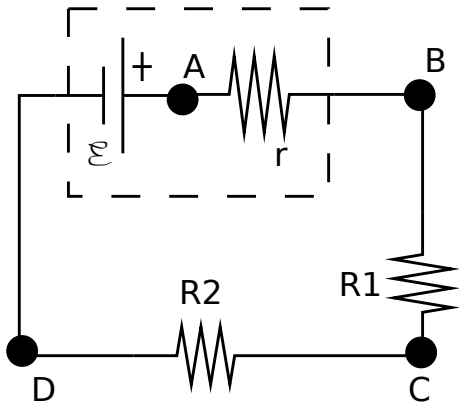
- (A) A
- (B) B
- (C) C
- (D) D
- (E) A and B (they are the same)



A: Real battery and two resistors in series II

Given that definition of $V = 0$, at what point is the electric potential the largest?


- (A) A
- (B) B
- (C) C
- (D) D
- (E) E

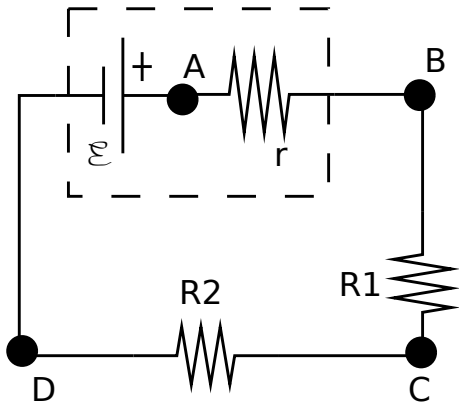

Q: Real battery and two resistors in series III

Where is the current the largest?

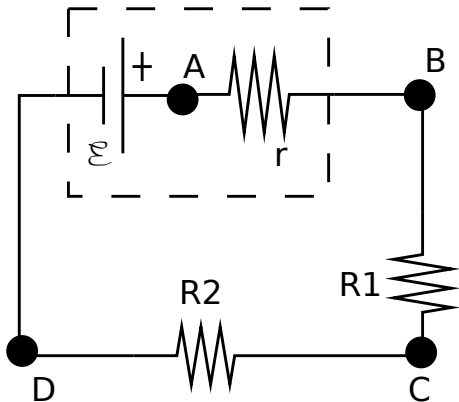
- (A) A
- (B) B
- (C) C
- (D) D
- (E) A and B (they are the same)
- (F) It is the same at all points



A: Real battery and two resistors in series III

Where is the current the largest?

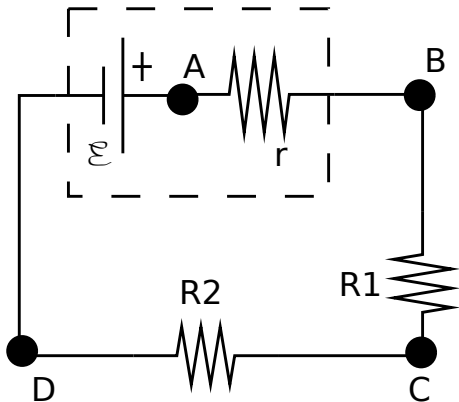
- (A)
- (B)
- (C)
- (D)
- (E)
- (F) It is the same at all points



Q: Real battery and two resistors in series IV

Given these values, and our definition of $V = 0$ at point D , what is the potential at point B ?
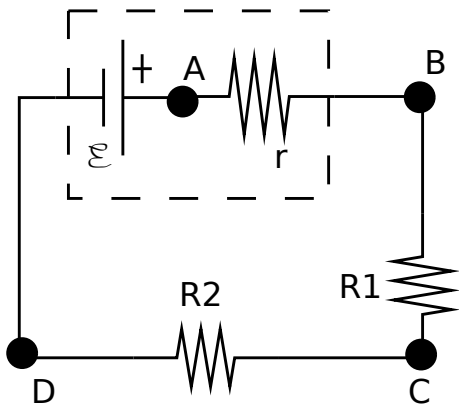
$$\mathcal{E} = 28\text{V}, I = 2\text{A}$$
$$r = 3\Omega, R_1 = 6\Omega$$



A: Real battery and two resistors in series IV

Given these values, and our definition of $V = 0$ at point D , what is the potential at point B ?

$$V_A = +28V$$


$$V_A - V_B = Ir$$

$$V_B = V_A - Ir$$

$$V_B = +28 - (2)(3)$$

$$V_B = 22V$$

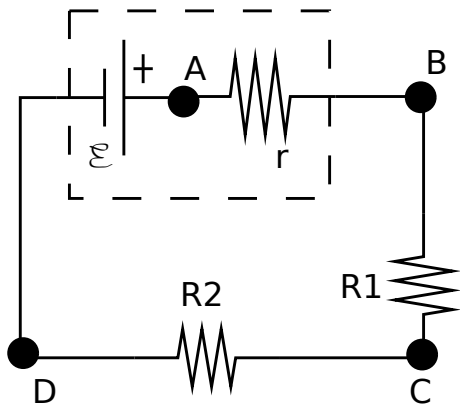
$$\mathcal{E} = 28V, I = 2A$$
$$r = 3\Omega, R_1 = 6\Omega$$



Q: Real battery and two resistors in series V

What is the potential *difference*
 $V_A - V_C$ in terms of I , r , and R_1 ?
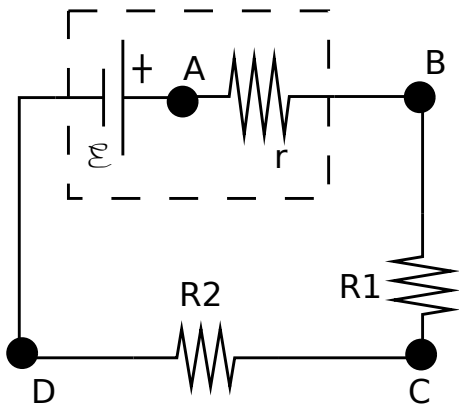
$$\mathcal{E} = 28\text{V}, I = 2\text{A}$$
$$r = 3\Omega, R_1 = 6\Omega$$



A: Real battery and two resistors in series V


What is the potential *difference*
 $V_A - V_C$ in terms of I , r , and R_1 ?

$$\mathcal{E} = 28\text{V}, I = 2\text{A}$$
$$r = 3\Omega, R_1 = 6\Omega$$


$$V_A - V_C = I(r + R_1) = 18\text{V}$$

This is a general result. Any number
of resistors in series behaves as a
single resistor of *equivalent*
resistance:

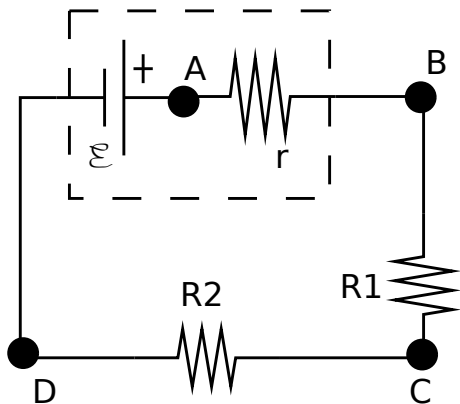
$$R_{\text{series}}^{\text{tot}} = \sum R_i$$




Series and Parallel Resistors

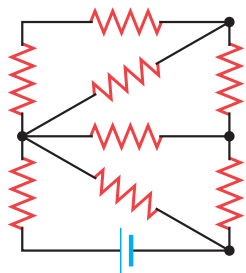

(a)

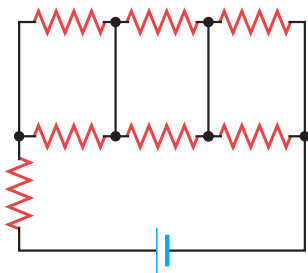


(b)

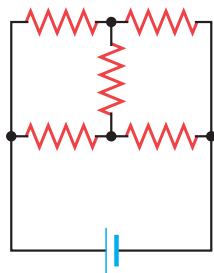


(c)

Which of the above circuits do not have any resistors in series or in parallel?


Series and Parallel Resistors

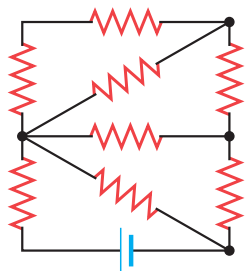

(a)

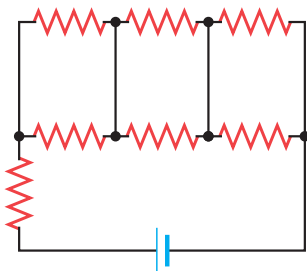

(b)

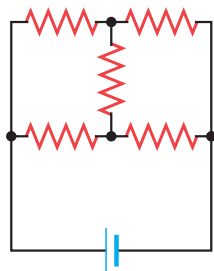

(c)

Which of the above circuits do not have any resistors in series or in parallel?

Circuit (C) does not have any resistors in series or parallel.

- **Junction Rule:** At a junction in a circuit, the sum of the currents flowing into the junction equals the sum of the currents flowing out of the junction.

$$\sum_{\text{junction}} i_k = 0 \quad (1)$$

Kirchhoff's Rules

- **Junction Rule:** At a junction in a circuit, the sum of the currents flowing into the junction equals the sum of the currents flowing out of the junction.

$$\sum_{\text{junction}} i_k = 0 \quad (1)$$

- **Loop Rule:** The sum of all of the potential drops and rises around a closed loop is equal to zero.

$$\sum_{\text{loop}} V_k = 0 \quad (2)$$

Junction Rule

- The total current that flows into a junction is equal to the total current that flows out of a junction.

Junction Rule

- The total current that flows into a junction is equal to the total current that flows out of a junction.
- Since charge must be conserved, any charge that flows into a junction must flow out.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when
 - Going from the negative terminal of a battery to the positive.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when
 - Going from the negative terminal of a battery to the positive.
 - Going over a resistor in the direction opposite of our defined current.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when
 - Going from the negative terminal of a battery to the positive.
 - Going over a resistor in the direction opposite of our defined current.
- We get a potential drop when

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when
 - Going from the negative terminal of a battery to the positive.
 - Going over a resistor in the direction opposite of our defined current.
- We get a potential drop when
 - Going from the positive terminal of a battery to the negative.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when
 - Going from the negative terminal of a battery to the positive.
 - Going over a resistor in the direction opposite of our defined current.
- We get a potential drop when
 - Going from the positive terminal of a battery to the negative.
 - Going over a resistor in the direction we have defined our current.

Loop Rule

- The sum of all of the potential drops and rises around a closed loop is equal to zero.
- Everywhere in the circuit we begin by assigning current directions.
- We then chose a starting point and go around the loop adding all the potential drops and rises.
- We get a potential rise when
 - Going from the negative terminal of a battery to the positive.
 - Going over a resistor in the direction opposite of our defined current.
- We get a potential drop when
 - Going from the positive terminal of a battery to the negative.
 - Going over a resistor in the direction we have defined our current.
- There are generally extra loops that are just combinations of the other loops. These provide no additional information and can be ignored.

Solving Problems with Kirchhoff's Rules

1. Draw the circuit diagram and label everything you know and don't know.

Solving Problems with Kirchhoff's Rules

1. Draw the circuit diagram and label everything you know and don't know.
2. Randomly assign a direction for each of the unknown currents and draw them on your diagram. If you get the direction wrong, you will simply get a negative current.

Solving Problems with Kirchhoff's Rules

1. Draw the circuit diagram and label everything you know and don't know.
2. Randomly assign a direction for each of the unknown currents and draw them on your diagram. If you get the direction wrong, you will simply get a negative current.
3. Identify each junction and apply the junction rule to each.

Solving Problems with Kirchhoff's Rules

1. Draw the circuit diagram and label everything you know and don't know.
2. Randomly assign a direction for each of the unknown currents and draw them on your diagram. If you get the direction wrong, you will simply get a negative current.
3. Identify each junction and apply the junction rule to each.
4. Count your unknowns and if you need more equations, define a loop. Randomly chose a direction you will travel along your loop. Draw this on your diagram.

Solving Problems with Kirchhoff's Rules

1. Draw the circuit diagram and label everything you know and don't know.
2. Randomly assign a direction for each of the unknown currents and draw them on your diagram. If you get the direction wrong, you will simply get a negative current.
3. Identify each junction and apply the junction rule to each.
4. Count your unknowns and if you need more equations, define a loop. Randomly chose a direction you will travel along your loop. Draw this on your diagram.
5. Go around each loop in your assigned direction calculating the rises and drops in potential as you go.

Solving Problems with Kirchhoff's Rules

1. Draw the circuit diagram and label everything you know and don't know.
2. Randomly assign a direction for each of the unknown currents and draw them on your diagram. If you get the direction wrong, you will simply get a negative current.
3. Identify each junction and apply the junction rule to each.
4. Count your unknowns and if you need more equations, define a loop. Randomly chose a direction you will travel along your loop. Draw this on your diagram.
5. Go around each loop in your assigned direction calculating the rises and drops in potential as you go.
6. Repeat steps 4 and 5 until you have as many equations as unknowns and solve.